
 


CPE 470 - Accelerator Optimization

 

Sequential Logic


- Many operations can be expressed as smaller sequential steps
 - Ex: Multiplication as multiple steps of addition
- Can use sequential algorithms to minimize logic usage and critical path
 - Sequential Multiplier uses one adder → shorter critical path
 - Much less area (one adder compared to N adders)
 - Tradeoff: now completes in a lot more cycles
 - 32 bit multiplier takes 32 cycles



Parallel Sequential

Throughput: how often an operation completes
Latency: how long an operation takes to complete from being started


- Sequential Algorithms often take much less area than their unrolled versions
 - Multiplication Example: 1 vs n adder modules for n bits
- Smaller area enables more parallelization: instantiate more of them
 - Queue and Dispatch operations as they come to available modules
 - Modules marked busy as they compute
- With enough parallel modules, throughput can scale
 - Example: With 1 32-bit sequential multiplier:
 - **Throughput** is 1 multiply every 32 cycles
 - **Latency** is 32 cycles (from dispatch to completion)
 - Example: With 32 32-bit sequential multipliers:
 - **Throughput** is 1 multiply every cycle
 - **Latency** is still 32 cycles

 

Pipelining

Pipelining: breaking a combinational path into steps by inserting registers

 
- What if we want to improve logic without having to switch to a purely sequential algorithm?
- Pipelining takes existing unrolled combinational block and divide it into steps
 - Each step should have a similar delay
 - Each step gets a register on its output
 - Each step's output register is the input to the next step



Breaking this logic into two stages brings total logic delay from 20 down to 10


- Pros:
 - Can introduce new data much faster, throughput is improved
 - With a balanced pipeline where every stage is equal delay, n-stages gives n-times the throughput
- Cons:
 - Latency is not improved
 - Registers cost area

Example: Multiplication

 


Pipelined Multiplication

 Idea: split processing across several clock cycles by dividing circuit into pipeline stages separated by registers that hold values passing from one stage to the next.



Pipelined Multiplication 2


★ = register

 

Multi Cycle Paths


Multi Cycle Path: combinational logic path that occurs over multiple clock cycles

- What if cannot break up an operation cleanly with flip flops?
 - Can't pipeline or sequentialize
- Use a **Multi Cycle Path**!
 - For an n-cycle path, only enable the input and output registers every n cycles
 - Benefits:
 - Can use logic with more delay than your clock period
 - Uses less synchronization registers
 - Drawbacks:
 - Does not get the improved throughput of pipelining
 - One computation at a time
 - Difficult to set up in STA
 - Easy to accidentally hide mistakes
- Example:
 - We want 2ns clock
 - Critical Path is 5ns
 - Use a 3-cycle path

 

Multi Cycle Path Clocking

 
- Multi Cycle Paths REQUIRE only activating registers every n cycles
 - Deciding something is a multi-cycle path is not enough
 - Have to manage timing manually with FSM, counters, or shift registers
- Example: 3 bit shift register activates flip flops every third cycle



Multicycle Path Timing

- Setup violations should only be checked N cycles out, when the output register is actually enabled
- Hold violations should only be checked during the launch cycle

Figure: Setup=5, Hold=4

 

Advanced Timing with SDCs

Glossary

SDC: Synopsys Design Constraints

- Basic Setup and Hold time violations are already handled by Openlane
- More advanced timing requires use of **SDC** Files
 - Originally from Synopsys, but now an industry standard
 - Xilinx's XDC format is very similar
 - Uses **TCL** language
- Allows defining special timing paths.
- Two main ways of interacting with design:
 - `[get_ports portname]`
 - gets one or more ports from the top level module of name
 - `[get_pins modulename/pinname]`
 - gets one or more pins, which is an input/output of an instantiated submodule

Create a clock signal named “clk” with T=10ns on the top-level port “clk”

Simulate the propagation delay of the clock more accurately

```
create_clock [get_ports clk] -name clk -period 10
set_propagated_clock clk
```

Multi Cycle Paths in SDCs

- Defined from the **Clock Pin** of the starting register to the **Data Input** pin of the ending register
- Setup path sets how many cycles
 - Example: Division takes ~165 ns, we want a clock period of 10ns
 - Set to a 17 cycle path
- Hold path should be one less than the setup path
- **Problem:** timing is done AFTER synthesis, on the gate-level netlist
 - Have to find signal names from your netlist (.nl.v file)
 - Use wildcard * to match all signals of a multi-bit vector

```
div Comb (.a_reg(a_reg), .b_reg(b_reg), .comb_out(comb_out));
```

```
set_multicycle_path -setup 17 -from [get_pins Comb.a_reg*/CLK ] -to [get_pins multicycle_out*df*/D]  
set_multicycle_path -hold 16 -from [get_pins Comb.a_reg*/CLK ] -to [get_pins multicycle_out*df*/D]
```

17 cycle path → 17 setup, 16 hold


Path starts at the clock pin of
the Comb module's a_reg pin

Path ends at the data pin of a
register outside the Comb module

False Paths

False Path: timing path that is never utilized

 - Sometimes designs will have critical paths that are not every actually used
- Timing tools don't know the state of muxes or logic; assume all paths are taken
 - **False Paths** are found by tools even though they are never reached at runtime
 - `set_false_path`
 - Similar syntax to multicycle paths from previous slides



- Example: design a module that multiply-adds or add-multiplies
 - Never double multiplies
- Critical path appears to be double multiply
 - Timing tool doesn't know which muxes are active or mutually exclusive
- Use false path to disable the unused path
 - Total delay is now $\text{delay}(+,*)$ rather than $\text{delay}(*,*)$

References

- <https://vlsitutorials.com/constraining-multi-cycle-path-in-synthesis/>
- <https://courses.csail.mit.edu/6.111/f2008/handouts/L09.pdf>
-